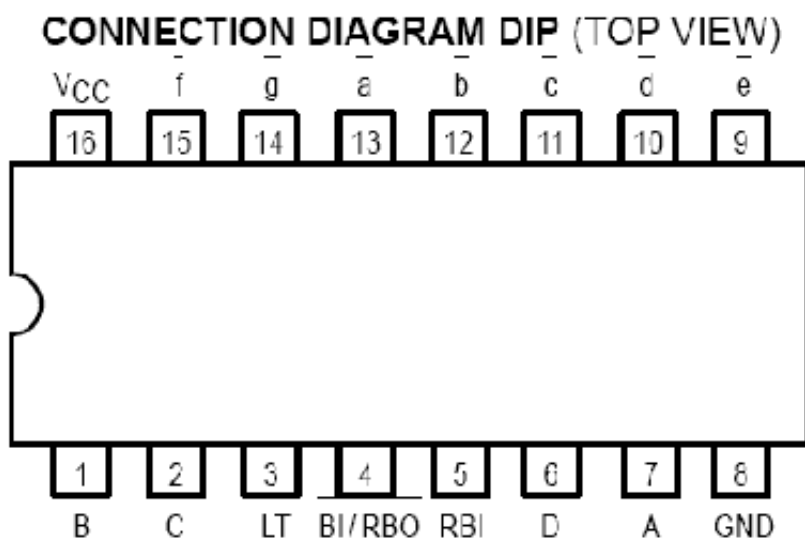


Using the 74xx47 BCD to Seven-segment display

The 74xx47 chip is used to drive 7 segment display. You must use the 74xx47 with a **common anode 7-segment display** (e.g. Kingbright part number SA03). The input to the 74xx47 is a binary number **DCBA** where D is 8s, C is 4s, B is 2s and A is 1s. The inputs DCBA often come from a binary counter.

The display is only sensible if the binary number is between DCBA=0000 (0) and DCBA=1001 (9); this is called Binary Coded Decimal or BCD for short. If the number is larger than 9 you get a strange output on the display. Try this out by moving your mouse over the truth table.


The inputs $\overline{\text{BI/RBO}}$, $\overline{\text{RBI}}$ and $\overline{\text{LT}}$ are usually connected to 5v



Simple use

1. Connect V_{cc} [pin 16], $\overline{\text{LT}}$ [pin 3], $\overline{\text{BI/RBO}}$ [pin 4] and $\overline{\text{RBI}}$ [pin 5] to 5v.
2. Connect Gnd [pin 8] to 0v.
3. connect DCBA [pins 1, 2, 6 and 7] to DCBA on your counter.
4. Connect $\overline{a}\overline{b}\overline{c}\overline{d}\overline{e}\overline{f}\overline{g}$ [pins 9-15] to abcdefg on the common anode 7-segment display.

Inputs							Outputs							
D	C	B	A	$\overline{\text{BI/RBO}}$	$\overline{\text{RBI}}$	$\overline{\text{LT}}$	\overline{a}	\overline{b}	\overline{c}	\overline{d}	\overline{e}	\overline{f}	\overline{g}	Display
0	0	0	0	1	1	1	0	0	0	0	0	0	1	
0	0	0	1	1	1	1	1	0	0	1	1	1	1	
0	0	1	0	1	1	1	0	0	1	0	0	1	0	
0	0	1	1	1	1	1	0	0	0	0	1	1	0	
0	1	0	0	1	1	1	1	0	0	1	1	0	0	
0	1	0	1	1	1	1	0	1	0	0	1	0	0	
0	1	1	0	1	1	1	1	1	0	0	0	0	0	

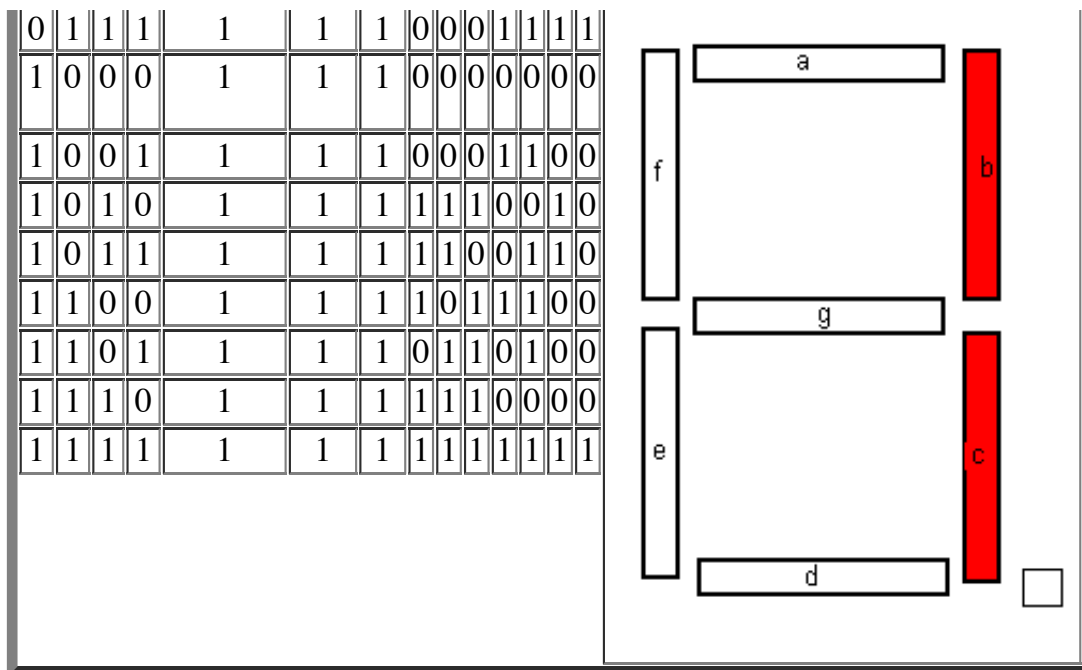

Advanced use

$\overline{\text{LT}}$ stands for Lamp Test. When $\overline{\text{LT}}$ is low all the segments on the 7-seg display are lit regardless of DCBA. [Click here to try this out on the truth table below.](#)

$\overline{\text{BI}}$ stands for Blanking Input. When $\overline{\text{BI}}$ is low the display is blank so all the segments on the 7seg display are off regardless of DCBA. [Click here to try this out on the truth table below.](#)

$\overline{\text{RBI}}$ stands for Ripple Blanking Input. When $\overline{\text{RBI}}$ is low and DCBA=0000 the display is blank otherwise the number is displayed on the display. This is used to remove leading zeroes from a number (e.g. display 89 instead of 089). To use with more than one display connect $\overline{\text{RBO}}$ (Ripple Blanking Output) from most significant 74xx47 to the $\overline{\text{RBI}}$ of the next 74xx47.

Connect $\overline{\text{RBI}}$ of the least significant 74xx47 to 5v unless you want the display to turn off when the number is 0.

Inputs							Outputs									
D	C	B	A	$\overline{\text{BI/RBO}}$	$\overline{\text{RBI}}$	$\overline{\text{LT}}$	a	b	c	d	e	f	g	Display		
X	X	X	X	0	1	1	1	1	1	1	1	1	1			
X	X	X	X	1	1	0	0	0	0	0	0	0	0			
0	0	0	0	1	0	1	1	1	1	1	1	1	1			
0	0	0	1	1	0	1	1	0	0	1	1	1	1			
0	0	1	0	1	0	1	0	0	1	0	0	1	0			
0	0	1	1	1	0	1	0	0	0	0	1	1	0			
0	1	0	0	1	0	1	1	0	0	1	1	0	0			
0	1	0	1	1	0	1	0	1	0	0	1	0	0			
0	1	1	0	1	0	1	1	1	0	0	0	0	0			
0	1	1	1	1	0	1	0	0	0	1	1	1	1			

1	0	0	0	1	0	1	0	0	0	0	0	0	0
1	0	0	1	1	0	1	0	0	0	1	1	0	0
1	0	1	0	1	0	1	1	1	1	0	0	1	0
1	0	1	1	1	0	1	1	1	0	0	1	1	0
1	1	0	0	1	0	1	1	0	1	1	1	0	0
1	1	0	1	1	0	1	0	1	1	0	1	0	0
1	1	1	0	1	0	1	1	1	1	0	0	0	0
1	1	1	1	1	0	1	1	1	1	1	1	1	1

a

b

c

d

e

f

g